

Course and Section _____

Names _____

Date _____

DC CIRCUITS PH106 EXPERIMENT

Introduction

In this experiment you will determine how voltages and current are distributed resistors circuits. In this experiment you explore how voltages and charges are distributed in a capacitor circuit. Resistor can be connected in several ways: in this experiment we study the series and the parallel combinations. You will also examine the charging of a capacitor in a RC circuit.

Equipment

Power supply, Multimeter, three 470Ω , one 1000Ω , one $12.4 \text{ k}\Omega$, one unknown (brown) resistors, one $2200 \mu\text{F}$ polar capacitor, five cables.

Theory

Resistors are electronic devices with fixed value of resistance R . The resistance R depends on the physical and geometrical proprieties of the device and is given operationally by the Ohm Law which states that the amount of current I passing through a resistor is directly proportional to the voltage difference across it.

$$I = \frac{\Delta V}{R}$$

The schematic symbol of a resistor or is




Series

In a series connection the components are connected at a single point, end to end.

When the series combination is connected to a power supply ΔV , the currents on each resistors I_1, I_2 are equal to current I through the equivalent resistor R . The potential difference across each resistor add to ΔV

$$I = I_1 = I_2$$

$$\Delta V = \Delta V_1 + \Delta V_2$$

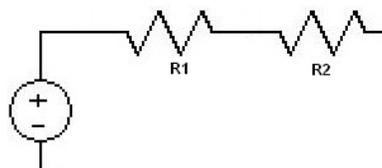

The equivalent R is

$$R = R_1 + R_2$$

Parallel


When the parallel combination is connected to a power supply ΔV , the currents on each resistors I_1, I_2 add to the current I through the equivalent resistor R . The potential difference across each resistor are equal to the potential difference ΔV .

$$I = I_1 + I_2$$

$$\Delta V = \Delta V_1 = \Delta V_2$$

The equivalent resistance R is
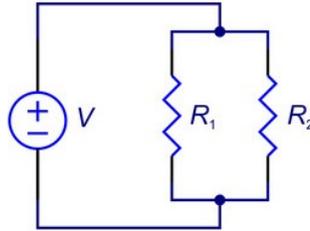
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$



Preliminary questions

You have three identical resistors. You connect two of them in series and to a 12 V power supply. If you add the third resistor in series with the others two.

1. How does the voltage across the first two resistors changes?
2. How does the equivalent resistance change?
3. How does the current through the first two resistors change?

You have three identical resistors. You connect two of them in parallel and to a 12 V power supply. If you add the third resistors in parallel with the others two.

4. How does the voltage across the first two resistor changes?
5. How does the equivalent resistance change?
6. How does the current through the first two resistors change?

PART 1 – Resistor combinations


Procedure

Step 1. Turn on the power supply and set the DC voltage to 10 V.

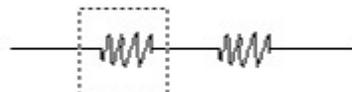7. Measure the actual power supply voltage V_{PS} with the multimeter and record it below

$$V_{PS} = \text{_____} \text{V}$$

Step 2. Connect two 470 Ω resistors in series.



8. Measure V_1 across R_1 (the resistor in the dashed box) and record it below.

$$V_1 \text{ (measured)} = \text{_____ V}$$

Next, you want to compute the expected value of V_1 by using the given equations

9. Calculate the equivalent resistance R_{12}

10. Calculate the total current I

11. Calculate the expected value of V_1

$$V_1 \text{ (expected)} = \text{_____ V}$$

12. Calculate the percentage error (assuming the exact value = measured value) of V_1

$$\% \text{ error} = (|\text{measured} - \text{expected}| / \text{measured}) \times 100 = \text{_____}$$

Step 3. Connect the unknown resistor R_2 (brown with no color code) in series with the $R_1 = 470 \Omega$ resistor and to the power supply. By taking measurements of voltage is possible to find the resistance of the unknown resistor.

13. Measure the voltages across each resistor

$$V_1 \text{ (measured)} = \text{_____ V,}$$

$$V_2 \text{ (measured)} = \text{_____ V,}$$

14. Calculate the resistance of R_2 using the values of V_1 , V_2 and R_1 . Think about the value of the current I through each resistors.

$$R_2 \text{ (expected)} = \text{_____ } \Omega.$$

15. Use the multimeter to measure the resistance of the unknown resistor

$$R_2 \text{ (measured)} = \text{_____ } \Omega.$$

16. Calculate the percentage error assuming the exact value = R_2 (measured)

$$\% \text{ error} = (|\text{measured} - \text{expected}| / \text{measured}) \times 100 = \text{_____}$$


Step 4. Connect three 470Ω resistors in series and measure the voltage across each resistor.

17. Are your results consistent with your prediction 1?

Step 5. Connect three 470Ω resistors in parallel and measure the voltage across each resistor.

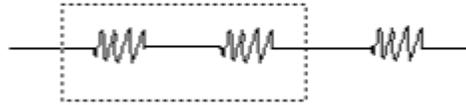18. Are your results consistent with your prediction 4?

Step 6. Connect two 470 Ω resistors and the 1000 Ω resistors in series, put the 1000 Ω in the middle.



19. Measure the voltage across the box $V_{BOX} = V_{12}$.

$$V_{12} \text{ (measured)} = \text{_____ V,}$$

Next, you want to compute the expected value of V_{12} using the given equations.

20. Calculate the equivalent resistance R_{12}

21. Calculate the equivalent resistance R_{123} .

22. Calculate the total current I

23. Given I , what is the value of the current I_{12} ?


24. By knowing R_{12} calculate the expected value of the voltage across the box

$$V_{12} \text{ (expected)} = \text{_____ V}$$

25. Calculate the percentage error of V_{12}

$$\% \text{ error} = (|\text{measured} - \text{expected}| / \text{measured}) \times 100 = \text{_____}$$

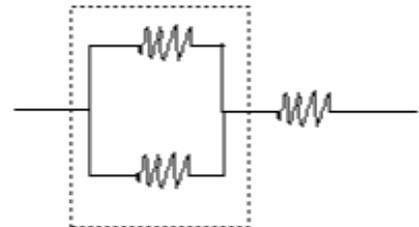Step 7. Remove the 1000 Ω resistor. Connect three 470 resistors as shown into the figure (to the right) and to the power supply.



26. Measure the voltage across the box $V_{BOX} = V_{12}$.

$$V_{12} \text{ (measured)} = \text{_____ V,}$$

Next, you want to compute the expected value of V_{12} by using the given equations.

27. Calculate the equivalent resistance R_{123} .

28. Calculate the total current I

29. Calculate the voltage across V_3 (by knowing I_3 and R_3)

30. By knowing V_{PS} and V_3 calculate the expected value of the voltage across the box

$$V_{12} \text{ (expected)} = \text{_____ V}$$

31. Calculate the percentage error of V_{12}

$$\% \text{ error} = (|\text{measured} - \text{expected}| / \text{measured}) \times 100 = \text{_____}$$

34. Use the multimeter to measure the resistance of the resistor. $R =$ _____

35. The capacitor has capacitance of about $C = 2200 \mu\text{F}$. Calculate the time constant

$$\tau = RC = \text{_____ (s)}$$

36. When $t = \tau$ the value of V_C should be about 63% of V_{PS} , that means $V_C = 0.63 \times 8.0 \text{ V} = 5.0 \text{ V}$. By looking at your data, does V_C reach 5.0V in about the time interval given by τ ?

If not, you might have to repeat *Step 2 – Step 4* to collect better data.

37. Plot your data in semi log format: $\ln(1 - V_C/V_{PS})$ on the vertical axis and t on the horizontal axis. How is the slope of this plot related to R and C ? Show your calculations.

38. What is the numerical value of the slope?

39. Print and submit a copy of your plot.

40. Use the value of the slope and of the resistance to estimate the capacitance.

$$C \text{ (measured)} = \text{_____ } \mu\text{F}$$

39. Calculate the percentage error, assuming the exact value $C = 2200 \mu\text{F}$

$$\% \text{ error} = (|\text{measured} - \text{exact}| / \text{exact}) \times 100 = \text{_____}$$

TURN OFF THE MULTIMETER and THE POWER SUPPLY